

# Low-Power System Design

## Final Exam (Take Home) Report


Ali Negary  
99721081

## Question 1)

- Design an 8x8 array multiplier using VHDL/Verilog.
- Synthesis your design using your desirable synthesis tool using 45nm technology.
- Report occupation area, power consumption, and delay of the design.
- Apply the pipelining technique to your design to reduce the power consumption and report the amount of power saving you have gained.
 
### Answer:

For the implementation of a simple 8\*8 array multiplier I utilized the following design.




a)

You can find the corresponding VHDL code in the directory *Question1/Multiplier\_8\_8* under the name *simple\_multiplier*.

b)


The code has been synthesized successfully using Xilinx ISE design tool on Xilinx Spartan-6 simulation setup which uses the 45nm technology.

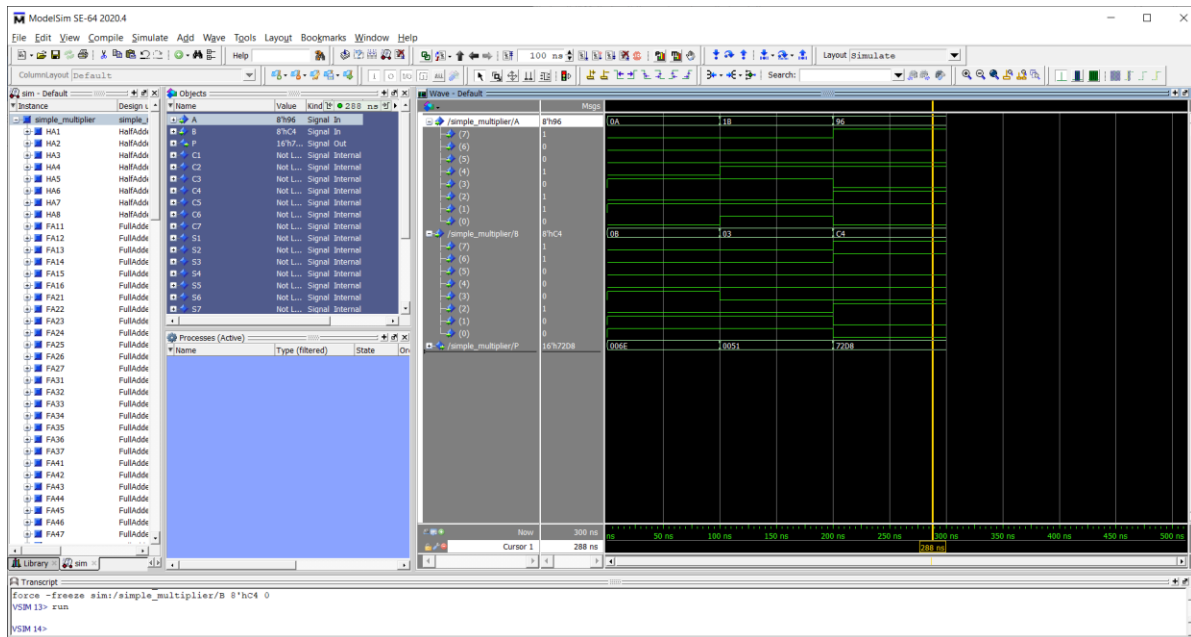Below, you can see the waveform of the output for 2 random inputs in the Modelsim simulator.



You can see the following test cases in the wave forms:

| A        | B        | P            |
|----------|----------|--------------|
| 0A (10)  | 0B (11)  | 006E (110)   |
| 1B (27)  | 03 (3)   | 0051 (81)    |
| 96 (150) | C4 (196) | 72D8 (29400) |

 

You can also find the ISE synthesis log from console in the same directory under the name *synthesis\_log.txt*.

c)

According to the synthesis report (you can find the report in *Question1/C\_Synthesis\_Report.txt*):

- 83 LUTs has been used out of 2400 LUTs on FPGA.
- 32 IOBs has been used out of 102 IOBs on FPGA.
- Critical Path has started in A1 and Finished in P14. The path has 18 levels of logic.
- Delay of Critical path has been estimated 20.349ns (34.7% logic, 65.3% route).
- Average Fan-out of Non-Clock Nets was 4.68.
- For power analysis, it seems like a face a hidden error. Xilinx Xpower runs without any warnings or errors but it only shows me power leakage (I gave up after 4 days of searching for this issue). So, leakage power consumption has the average of 0.014 Watts and maximum of 0.023 Watts.
- The supply and current analysis is shown below:

d)

Below, you can see the waveform of signal produced at each period of the VHDL code.

According to the synthesis report (you can find the report in *Question1/C Synthesis Report.txt*):

- Average Fan-out of Non-Clock Nets was 2.24.
- For power analysis, exact same issue with the other design. Code runs very well. It is compiled, synthesized, simulated, and the waveform is showing as it should. I thought maybe the issue is with the .vcd file that should be dumped by Xilinx Isim and I tried using Altera Modelsim. Unfortunately, the result is the same. Below are the commands I ran in Isim and the output file is the directory *Question1/Multiplier\_8\_8\_Pipeline* under the name *isim\_sim\_result.vcd* and *modelsim\_sim\_results.vcd*:

```

• ISim> vcd dumpfile isim_sim_result.vcd
• ISim> vcd dumpvars -m /
• ISim> vcd dumpon
• ISim>
• # isim force add {/pipeline_8x8/i_clk} 0 -radix bin -value 1 -radix bin -time 50
  ns -repeat 100 ns
• ISim>
• # isim force add {/pipeline_8x8/i_rstb} 1 -radix bin -cancel 20 ns
• ISim>
• # isim force add {/pipeline_8x8/i_ma} 01011011 -radix bin
• ISim>
• # isim force add {/pipeline_8x8/i_mb} 01110111 -radix bin
• ISim> run 1500 ns
• ISim> vcd dumpflush
• ISim>

```

#### Comparing the results)

Comparing result of Array design and Pipeline design, although the number of registers, LUTs, and IO block has increased (0 -> 107, 83 -> 107, and 32 -> 34), delays has been improved significantly from 20.34 to 4.901ns. Also fan-out has decline to half the amount of array design.

So, with 2.5 more area (including the register which were not used in the array design), we achieved more than 4 times speed-up (315%).


#### Question 2)

a) Design the 8x8 array multiplier in HSpice using 45nm technology (you can use Predictive Transistor Model: <http://ptm.asu.edu/>) and report the power consumption and the delay of your design.

b) Apply Dual-Vth technique to your design and report the power consumption and the delay. Please explain your observations and results in detail.
 
#### Answer:


To implement Array Multiplier, I benefited from the architecture from Question1. I have named the component as follow which matches the name of components in the netlist:



To design the gates and logical components I have utilized PTM models in my simulations.


a)

You can find the netlist and simulation results for this part of the question in the directory *Question2/Main\_Array\_Multiplier*. The designed multiplier has been tested with multiple static and dynamic scenarios of multiplying different numbers. The average power consumption and the delay of the circuit reported in the HSpice's report was 8.31 mWatts and 0.51 nSeconds. Power consumption has peaked nearly 12.96 mWatts and 7.79 mWatts at both ends. After stabilizing, the power peaks at 11.8 and 7.9. You can see a part of the power consumption in the diagram below.

 

b)

You can find the netlist and simulation results for this part of the question in the directory *Question2/Main\_Array\_Multiplier\_Dual\_Vth*. For benefiting the Dual Vth method, I have used the same transistor with changing the Vth in NMOS and PMOS each by 0.2 Volts. Higher Vth has been applied to the component which are not in the critical path (highlighted components in part a). The designed multiplier has been tested with exact scenarios as part a. The average power consumption and the delay of the circuit reported in the HSpice's report was 6.1 mWatts and the delay was still in the same range as reported in part a (although in 2 executions it exceeded for about 2-3%). Power consumption has peaked nearly 9.5 mWatts and 5.58 mWatts at both ends. You can see a part of the power consumption in the diagram below.

 

It seems like the delay has not increased, therefore the critical path is same as the part a. However, the power consumption has improved by 36% which is good news.

**Note1:** For question 2, all the components have been implemented and tested separately. You can find the results in the directory *Question2*.

**Note2:** I wrote the python script *net\_list\_writer.py* in Question2, to help me write the netlist. However, it does not provide everything.